

Aim: To study the load regulation and line regulation characteristics of Zener diode.

Apparatus: ① Zener diode.

② Resistor

③ Rheostat

④ Voltmeter

⑤ Ammeter

⑥ DC Source


⑦ Bread board

Theory: A Zener diode functions as an ordinary diode when it is forward biased. It is a specially designed device to operate in the reverse bias. When it is in the reverse breakdown region, the Zener voltage V_Z remains almost constant irrespective of the current I_Z through it. A series resistor R_S is used to limit the Zener current below its maximum current rating. The current through R_S is given by the expression $I_S = I_Z + I_L$, where I_L is the current through the load resistor R_L . The value of R_S must be properly selected to fulfill the following condition requirements.

When the input voltage, V_i increases I_L remains the same, I_S and I_Z increases. Similarly if input voltage decreases, I_L remains the same, I_S and I_Z decreases. But if I_Z falls lower than the

Teacher's Signature _____

Circuit Diagram:

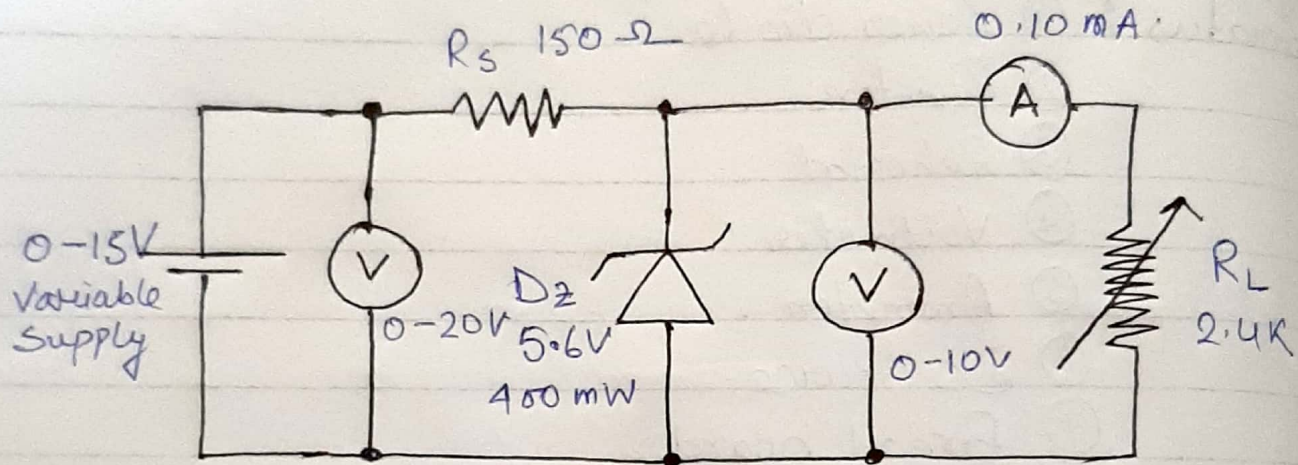

minimum zener current ~~through~~ enough to keep the zener in the breakdown region, the regulation will cease and output voltage decreases. A lower input voltage can cause the regulator fail to regulate. The series resistance should be selected between R_{smax} and R_{smin} which are given by the expression.

$$R_{smin} = [V_{i,max} - V_z] / I_{z,max}$$

$$R_{smax} = [V_{i,min} - V_z] / [I_{z,min} + I_L]$$

To Calculate percentage load regulation, mark V_{NL} and V_{FL} on Y-axis on the Load regulation graph. V_{NL} is the output voltage in the absence of load resistor and V_{FL} is the output voltage corresponding to rated I_L (here, 5mA). Calculate the percentage load regulation V_R as per the equation,

$$V_R = \frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\%$$

Calculation:-

Assume, $V_o = 5.6V$, $I_{max} = 5mA$ input voltage is in the range 8-14V.

Select 5.6V zener [$P_o = 400mW$, $V_z = 5.6V$, $r_d = 8\Omega$ at $I_z = 10mA$]

Use 2.4K rheostat as load resistance load current can be varied from 2.4mA and upwards.

Teacher's Signature _____

$$I_{2max} = \frac{P_{max}}{V_2} = \frac{0.4}{5.6} = 71.42 \text{ mA}$$

$$I_{2min} = 10\% \text{ of } I_{2max} = 0.1 \times 71.42 = 7.142 \text{ mA}$$

$$R_{smax} > R_s > R_{smin}$$

$$R_{smax} = \frac{[V_{imin} - V_2]}{[I_{2min} + I_{2max}]} \\ = \frac{(8 - 5.6)V}{(7.142 + 71.42) \text{ mA}} = 197.6 \Omega$$

$$R_{smin} = \frac{[V_{imax} - V_2]}{I_{2max}} \\ = \frac{(14 - 5.6)V}{71.42 \text{ mA}} = 117.6 \Omega$$

Select $R_s = 150 \Omega$.

Power Rating of R_s :-


$$\text{Max current through } R_s = I_m \\ = \frac{[V_{imin} - V_2]}{R_s} \\ = \frac{14 - 5.6 V}{150 \Omega}$$

$$= 56 \text{ mA}$$


$$\text{Power rating of } R_s = I_m^2 \times R_s \\ = 0.4704 \text{ W} >$$

Select 150 ohms
0.5 W resistor.

Teacher's Signature

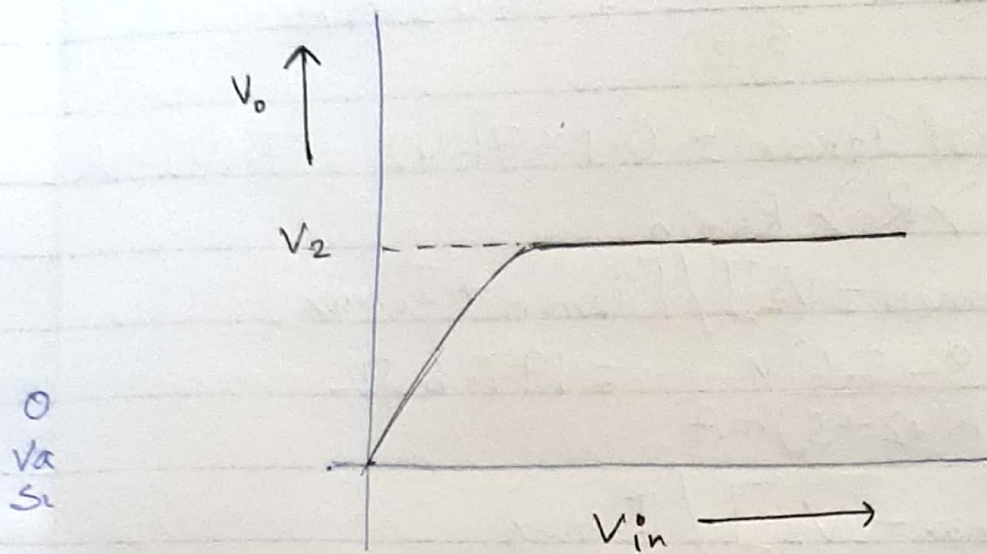

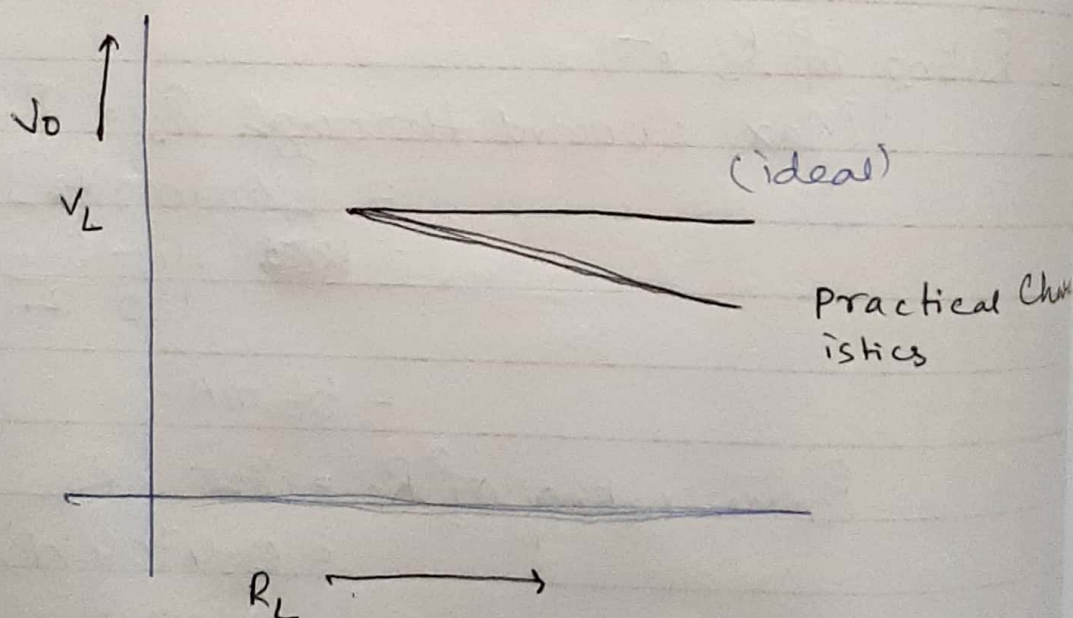Output Voltage vs. input voltage
for Line Regulation.



Output Voltage vs input voltage
for Load regulation.

Linear Regulation :

Keeping Load current constant at $I_L = 5 \text{ mA}$,
The input voltage is 8 to 14 V and corresponding
Observation are made.

V_{in}	V_o
8	5.60
10	5.60
12	5.60
14	5.60

Load Regulation :

Keeping input voltage at 10V, the Load current
is varied from 0 to 5 mA and observations are made.
For taking reading corresponding to no load ($I_L = 0$), the
Loading rheostat,

R_L	$I_L \text{ mA}$	$V_o \text{ (VOLT)}$
1250	4.48	5.60
1028	5.45	5.60
856	6.54	5.60
703	7.07	5.60

Teacher's Signature _____

Pre Cautions: ① All the connections should be proper, neat and clean.

② Polarity of devices should be checked.

③ Power should be turned off while construction of a circuit is in progress.

Teacher's Signature _____